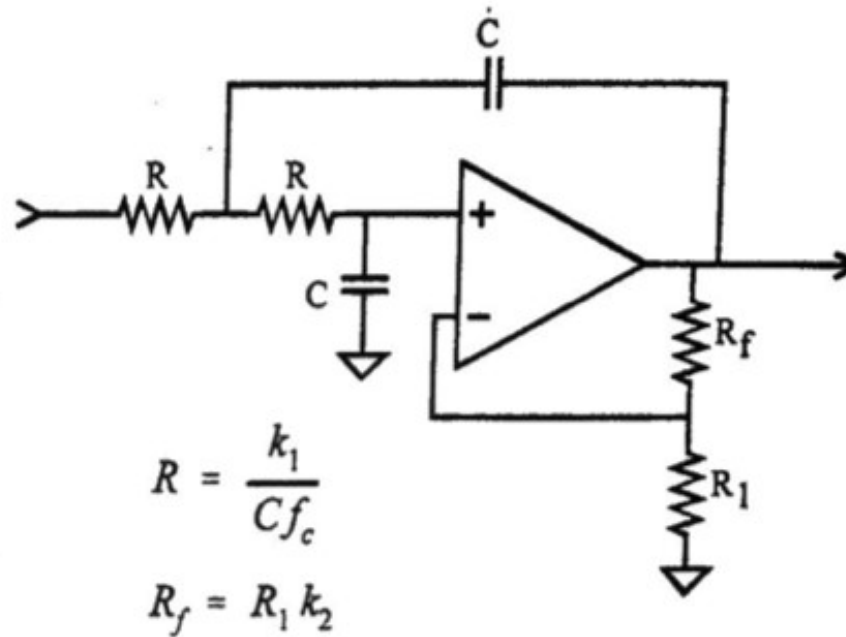





Active Filters





Ideal Low Pass Filter

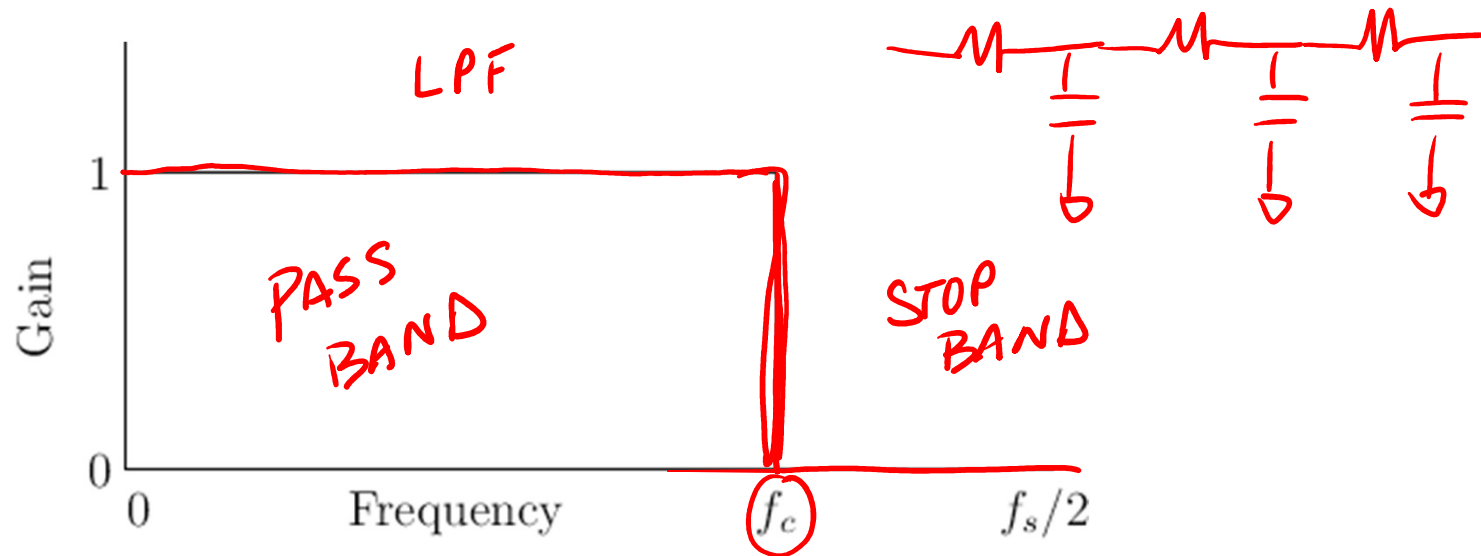


What is it that we want from a filter:

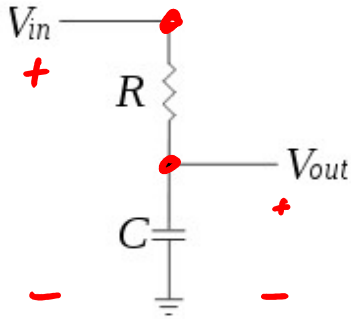- (1) Flat gain in the pass band
- (2) Low distortion in the pass-band (low or even phase shift)
- (3) Sharp corner and steep fall-off above the cut-off frequency

Low Pass Filter Revisted


$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$



$$\begin{aligned} \omega = 0 & \quad H(0) = 1 \\ \omega \rightarrow \infty & \quad H(\infty) \rightarrow 0 \end{aligned}$$

Bode diagram

1st Order
low pass
filter

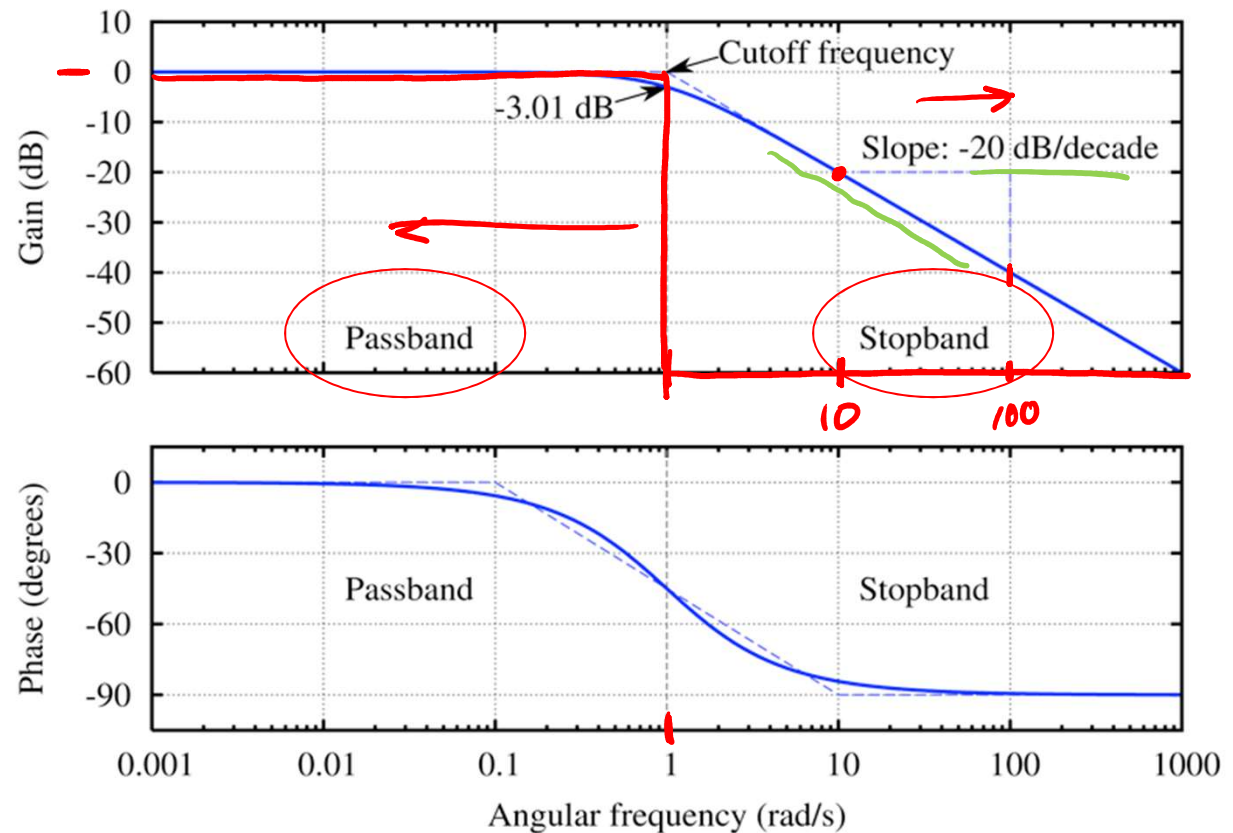

$$\omega_0 = 1 \text{ rad/sec}$$


Higher Order Filters

2nd Order Active Filter

- You can easily design a filter with -40 dB/decade
 - 1 Op-Amp, 2 Resistors and 2 Capacitors
 - Compare to -20 dB/decade 1 Resistor and 1 Capacitor

- Filter designs are available in the text book
 - Rarely necessary to design from scratch

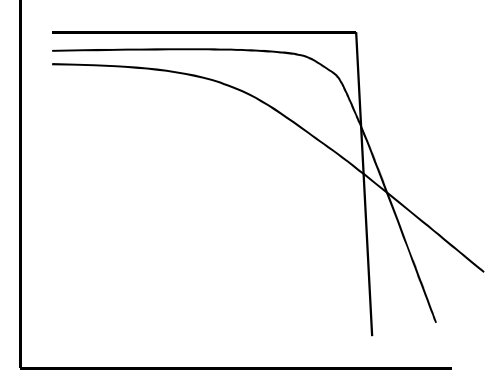- There are many filter designs
 - * Butterworth, Bessel, Chebyshev, etc.
- Some designs are flatter near the cutoff.





- We will examine more closely the Sallen-Key filter^f



Butterworth, Chebyshev, Bessel

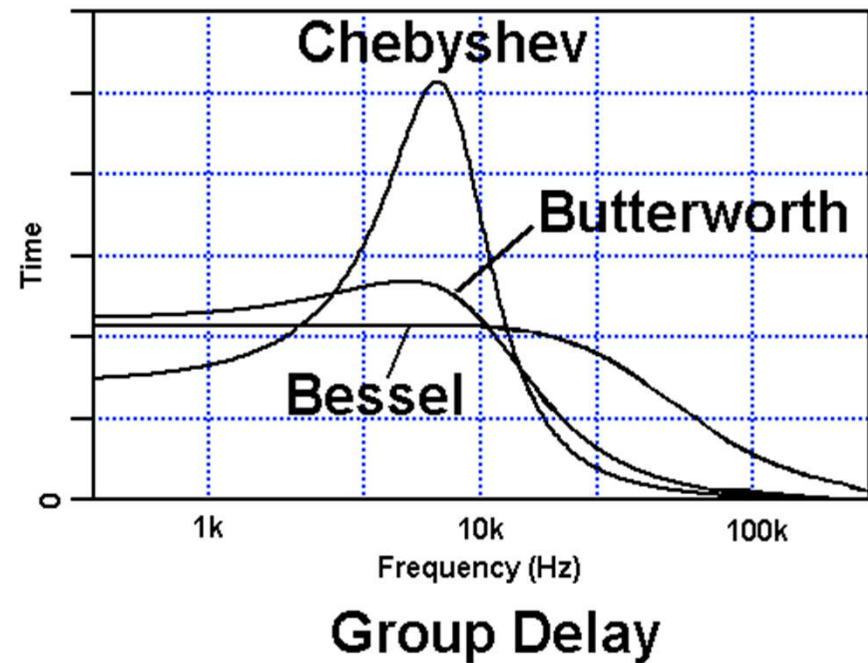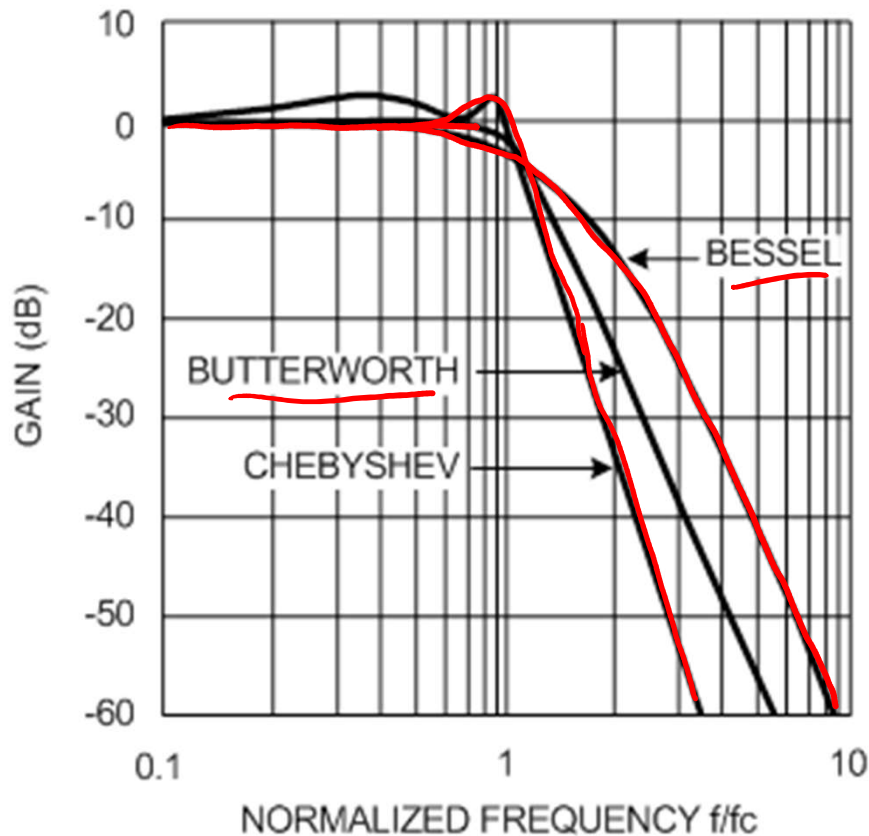
$C_1 = C_2 \Rightarrow$ Bessel
 $C_1 \neq C_2 \Rightarrow$ Chebyshev



Comparison of Gain Responses of Fourth Order Low Pass Filters



Order of filters (Butterworth)

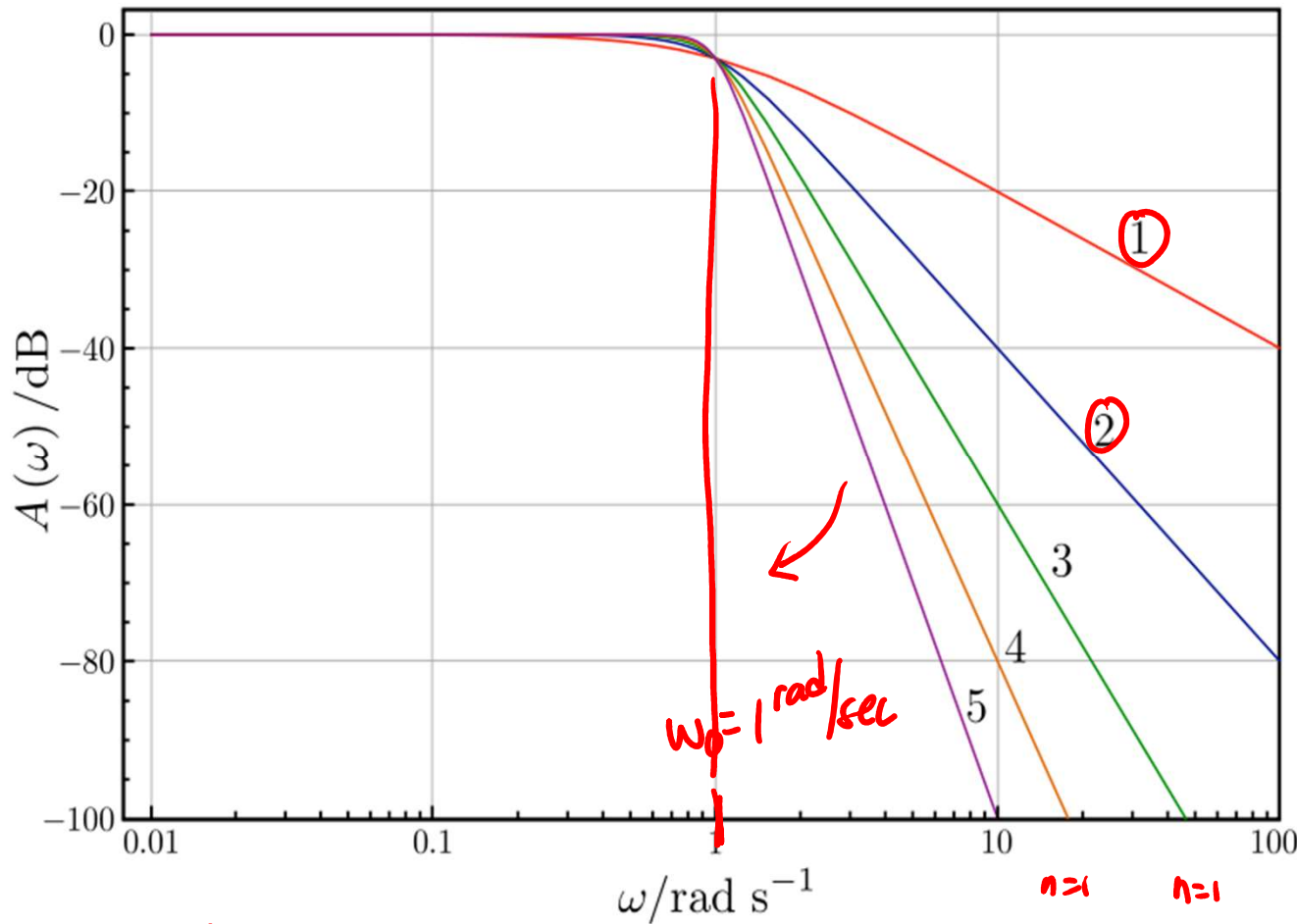

$$|H(\omega)| = 1 / (1 + \omega/\omega_0)^n$$



N = order of filter

N = 1 (-20dB/decade)

N = 2 (-40 dB/decade)


N = 5 (-100 dB/decade)

RC Filter $n=1$

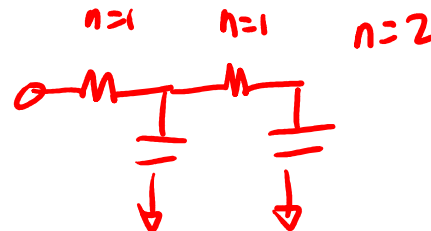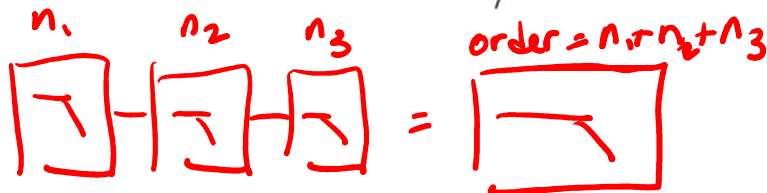



Sallen-Key 2nd Order Filter

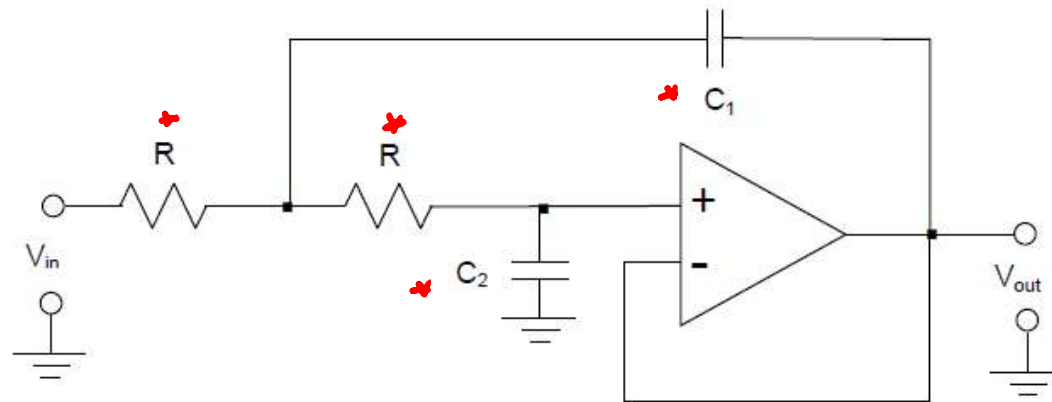

$$C_1 = 10C$$
$$C_2 = \frac{1}{10}C$$

$$\frac{V_{out}}{V_{in}} = \frac{\omega_o^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2}$$
$$\omega_o = \frac{1}{R\sqrt{C_1 C_2}}; Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$

$$C_1 = C_2$$
$$\omega_o = \frac{1}{RC}$$

$$C_1 = 10 \cdot C_2$$
$$C_1 = \underline{100C_2}$$


$$Q = \frac{1}{2}$$

$$Q = \frac{\sqrt{10}}{2} = \frac{3}{2} \approx 1.5$$

$$Q = \frac{10}{2} = 5$$



Sallen-Key Filter Derivation

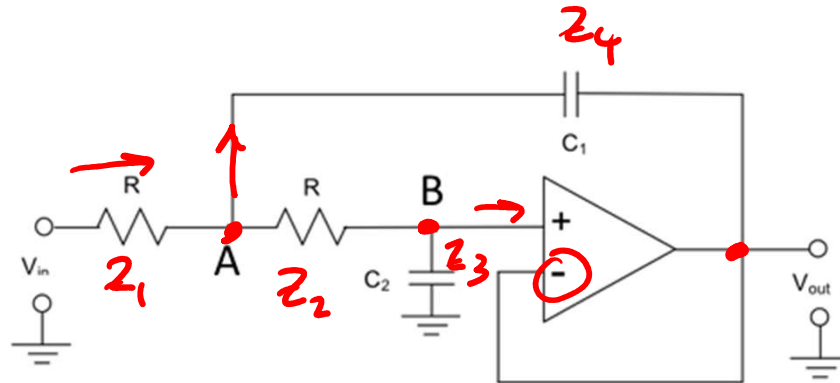

$$\underline{Z_1 = Z_2 = R}, \underline{Z_3 = 1/j\omega C_1}, \text{ and } \underline{Z_4 = 1/j\omega C_2}.$$

$$\underline{\frac{V_{in} - V_A}{Z_1}} = \frac{V_A - V_{out}}{\underline{Z_3}} + \frac{V_A - V_B}{\underline{Z_2}}$$

$$\underline{V_B = V_{out}}$$

$$\frac{V_A - V_{out}}{Z_2} = \frac{V_{out}}{Z_4}$$

- Revisiting op-amps
- Exploiting basic rules:
 - KCL
 - Op-Amp rule #1 ($V^+ = V^-$)
 - Op-Amp rule #2 ($i_{in} = 0$)



Sallen-Key Filter Transfer Function

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - (\omega^2 / \omega_0^2) + j(\omega / Q \omega_0)} = \frac{\omega_0^2}{\omega_0^2 - \omega^2 + j \frac{\omega_0}{Q} \omega}$$


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + \frac{\omega_0^2 \omega^2}{Q^2}}}$$

$$C_1 = C_2$$

$$Q = \frac{1}{2}$$

$$\omega_0^2 = (1/R^2 C_1 C_2)$$
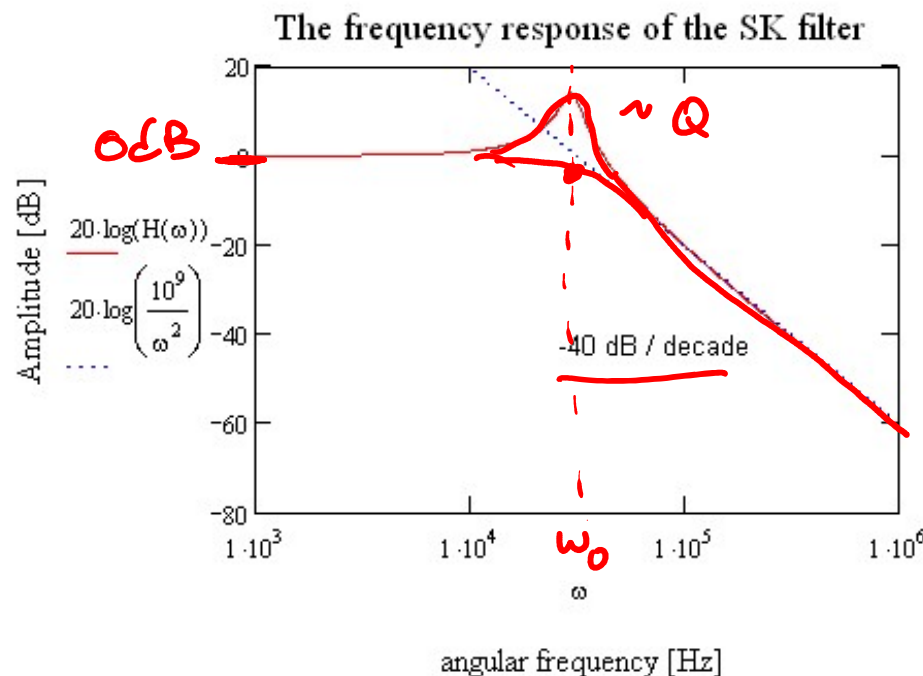
$$Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$



Observations

- Gain = 1 at DC & low freq.
- Gain = Q at $\omega = \omega_0$
- -40dB/decade stop band (2nd order filter)
- The SK filter is one of the options in the final practical



Cascaded Filters

6th order filter

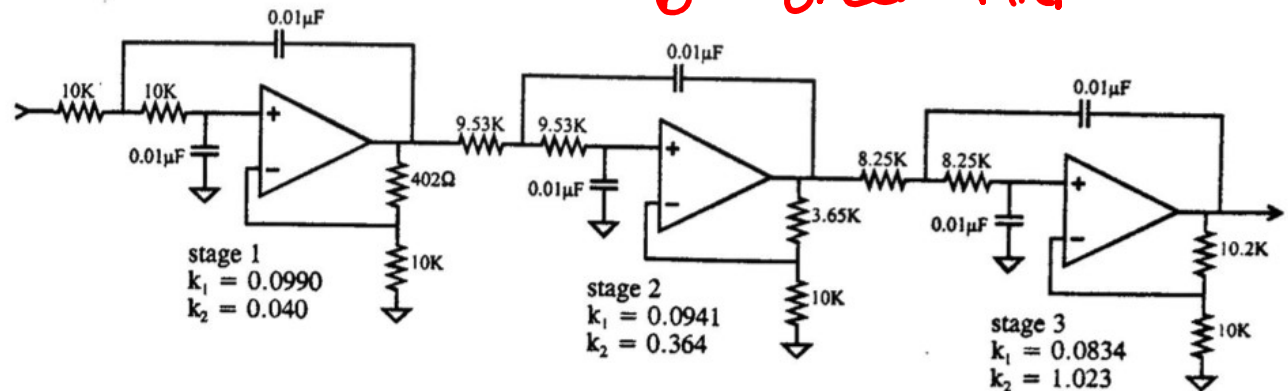
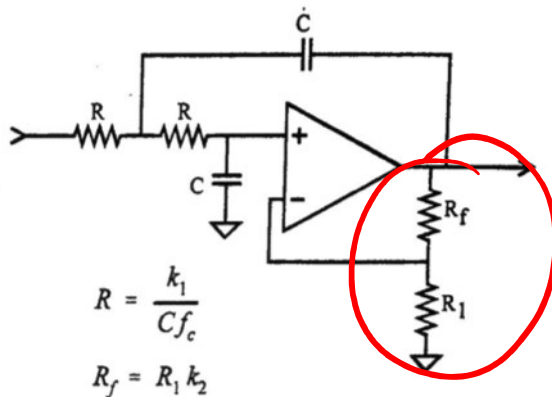


FIGURE 3-9

A six-pole Bessel filter formed by cascading three Sallen-Key circuits. This is a low-pass filter with a cutoff frequency of 1 kHz.


TABLE 3-1

Parameters for designing Bessel, Butterworth, and Chebyshev (6% ripple) filters.

# poles		Bessel		Butterworth		Chebyshev	
		k_1	k_2	k_1	k_2	k_1	k_2
2	stage 1	0.1251	0.268	0.1592	0.586	0.1293	0.842
4	stage 1	0.1111	0.084	0.1592	0.152	0.2666	0.582
	stage 2	0.0991	0.759	0.1592	1.235	0.1544	1.660
6	stage 1	0.0990	0.040	0.1592	0.068	0.4019	0.537
	stage 2	0.0941	0.364	0.1592	0.586	0.2072	1.448
	stage 3	0.0834	1.023	0.1592	1.483	0.1574	1.846
8	stage 1	0.0894	0.024	0.1592	0.038	0.5359	0.522
	stage 2	0.0867	0.213	0.1592	0.337	0.2657	1.379
	stage 3	0.0814	0.593	0.1592	0.889	0.1848	1.711
	stage 4	0.0726	1.184	0.1592	1.610	0.1582	1.913

- Bessel, Butterworth, Chebyshev filters can be constructed from Sallen-Key
- Multiple stages → higher order
- Generic filter design – Do not start from scratch!

Importance of filters in communication

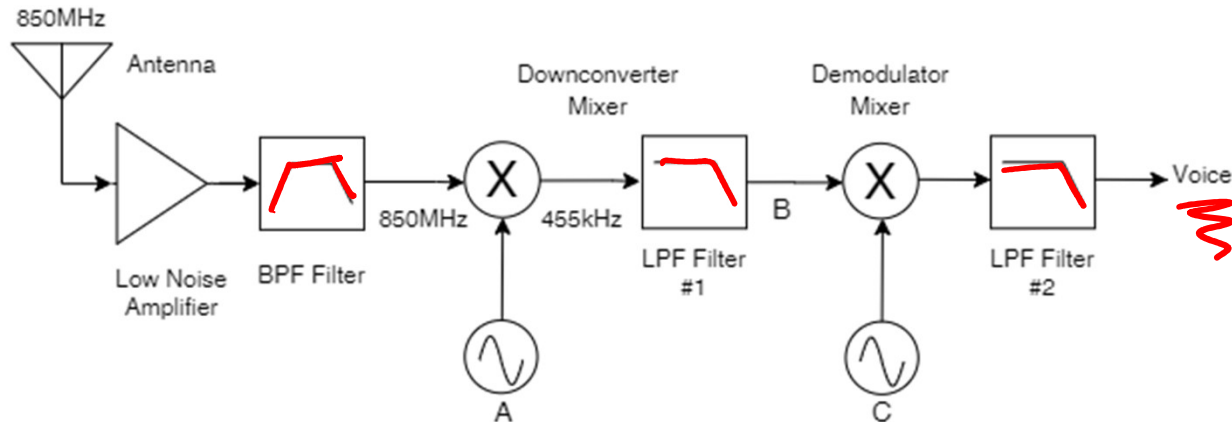

- Get rid of unwanted frequencies (e.g. harmonics generated in the mixing process)
- Limit the bandwidth (frequency range)
 - Bandwidth is precious
 - Stations/communication channels are closely packed
 - Need to avoid interference (overlap of stations)



Frequency Channelization

